

ECE 4263


Lab-6(B) Gate Family

Mukul Deshpande

Msd153

1)Schematics

C) DCVSL

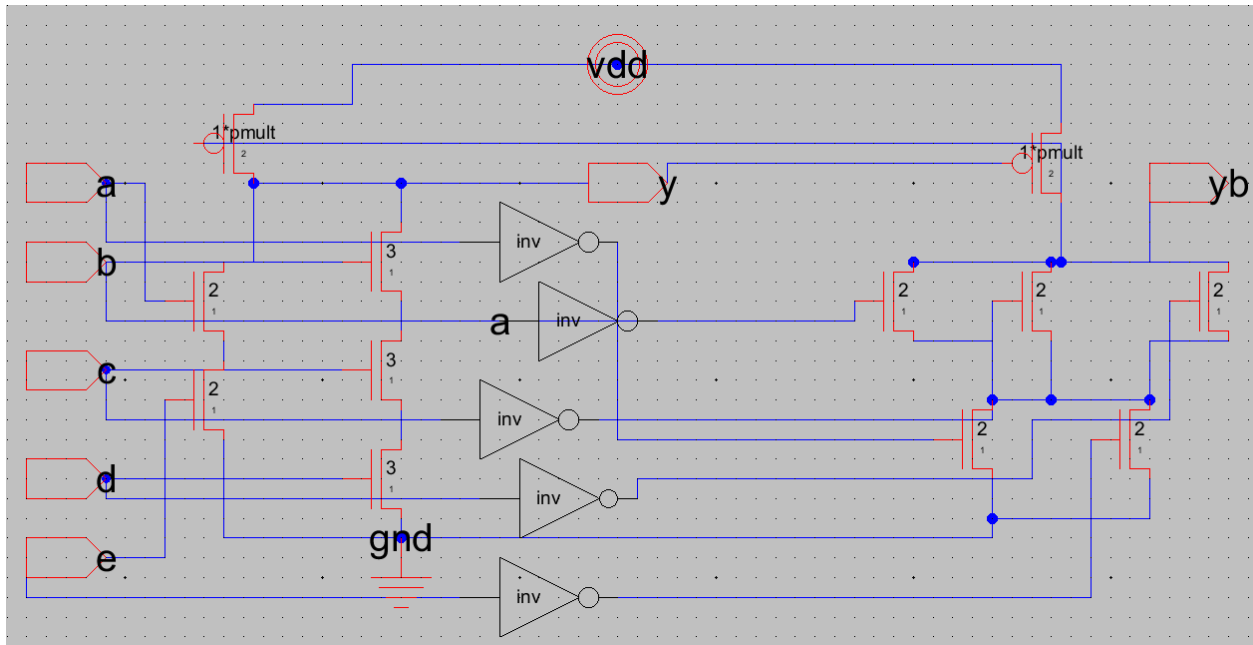


```

subckt dcvs1_gate (a b c d e y ab bb cb db eb yb vddc gndc)
  parameters size=1
  m1 (y a net29 gndc) n_def ws=2*size ls=1
  m2 (net29 e gndc gndc) n_def ws=2*size ls=1
  m3 (y b net28 gndc) n_def ws=3*size ls=1
  m4 (net28 c net27 gndc) n_def ws=3*size ls=1
  m5 (net27 d gndc gndc) n_def ws=3*size ls=1
  m6 (y yb vddc vddc) p_def ws=1*p_mult*size ls=2
  m7 (yb bb net26 gndc) n_def ws=2*size ls=1
  m8 (yb cb net26 gndc) n_def ws=2*size ls=1
  m9 (yb db net26 gndc) n_def ws=2*size ls=1
  m10 (net26 ab gndc gndc) n_def ws=2*size ls=1
  m11 (net26 eb gndc gndc) n_def ws=2*size ls=1
  m12 (yb y vddc vddc) p_def ws=1*p_mult*size ls=2
ends dcvs1_gate

```

D) dual_rail_domino

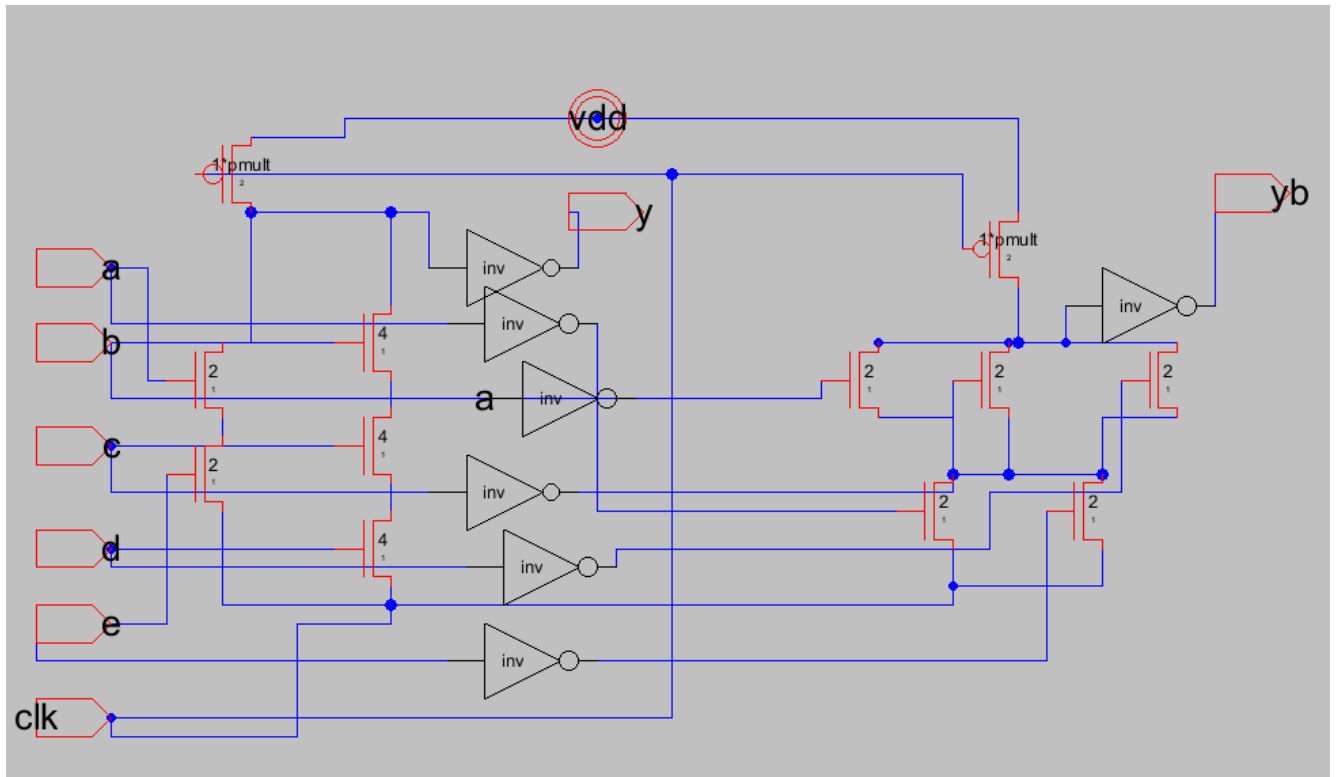

```

subckt dual_rail_domino_gate (clk a b c d e y ab bb cb db eb yb vddc gndc)
  parameters size=1
  x1 (net25 y vddc gndc) inv_gen size=1
  m1 (net25 a net29 gndc) n_def ws=5.35*size ls=1
  m2 (net29 e net24 gndc) n_def ws=5.35*size ls=1
  m13 (net24 clk gndc gndc) n_def ws=8*size ls=1
  m3 (net25 b net28 gndc) n_def ws=8*size ls=1
  m4 (net28 c net27 gndc) n_def ws=8*size ls=1
  m5 (net27 d net24 gndc) n_def ws=8*size ls=1
  m6 (net25 clk vddc vddc) p_def ws=1*p_mult*size ls=1
  x2 (net23 yb vddc gndc) inv_gen size=1
  m7 (net23 bb net26 gndc) n_def ws=5.35*size ls=1
  m8 (net23 cb net26 gndc) n_def ws=5.35*size ls=1
  m9 (net23 db net26 gndc) n_def ws=5.35*size ls=1
  m10 (net26 ab net24 gndc) n_def ws=5.35*size ls=1
  m11 (net26 eb net24 gndc) n_def ws=5.35*size ls=1
  m12 (net23 clk vddc vddc) p_def ws=1*p_mult*size ls=1
ends dual_rail_domino_gate


```

2) Truth_table


Case	A	B	C	D	E	Y=NOT(AE+BCD)
1	0	0	0	0	0	1
2	0	0	0	0	1	1
3	0	0	0	1	0	1
4	0	0	0	1	1	1
5	0	0	1	0	0	1
6	0	0	1	0	1	1
7	0	0	1	1	0	1
8	0	0	1	1	1	1
9	0	1	0	0	0	1
10	0	1	0	0	1	1
11	0	1	0	1	0	1
12	0	1	0	1	1	1
13	0	1	1	0	0	1
14	0	1	1	0	1	1
15	0	1	1	1	0	0
16	0	1	1	1	1	0
17	1	0	0	0	0	1
18	1	0	0	0	1	0
19	1	0	0	1	0	1
20	1	0	0	1	1	0
21	1	0	1	0	0	1
22	1	0	1	0	1	0
23	1	0	1	1	0	1
24	1	0	1	1	1	0
25	1	1	0	0	0	1
26	1	1	0	0	1	0
27	1	1	0	1	0	1
28	1	1	0	1	1	0
29	1	1	1	0	0	1
30	1	1	1	0	1	0
31	1	1	1	1	0	0
32	1	1	1	1	1	0

2) Waveforms

C) DCVSL

 

D) Dual rail domino

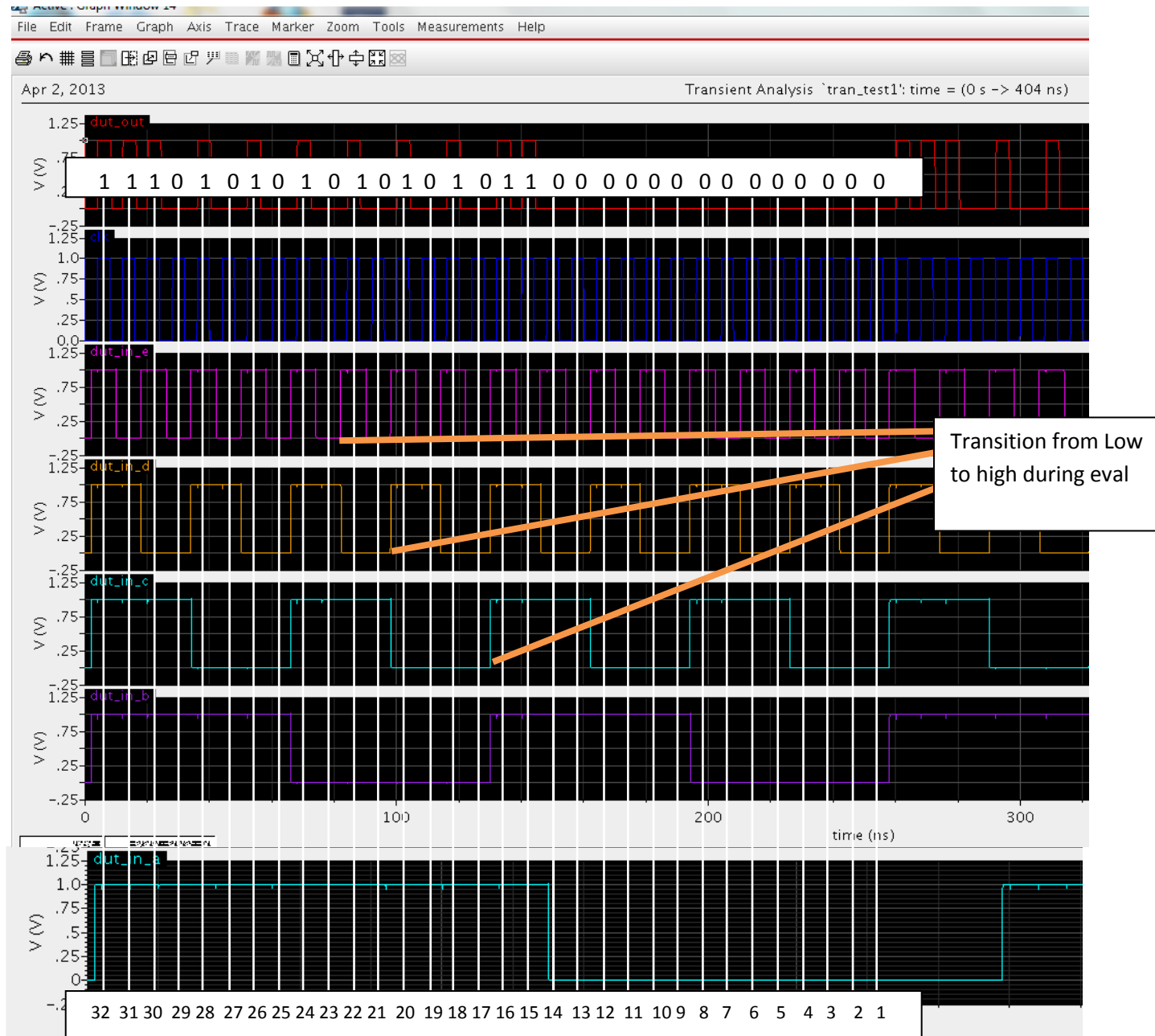

4)) I spent around 19-20 hours on this lab.